

---

# **A Novel Digital Hysteresis Current Controller for an Active Power Filter**

---


**D.M.E. Ingram & S.D. Round**

Department of Electrical & Electronic Engineering  
University of Canterbury  
Christchurch, New Zealand

# The Active Power Filter
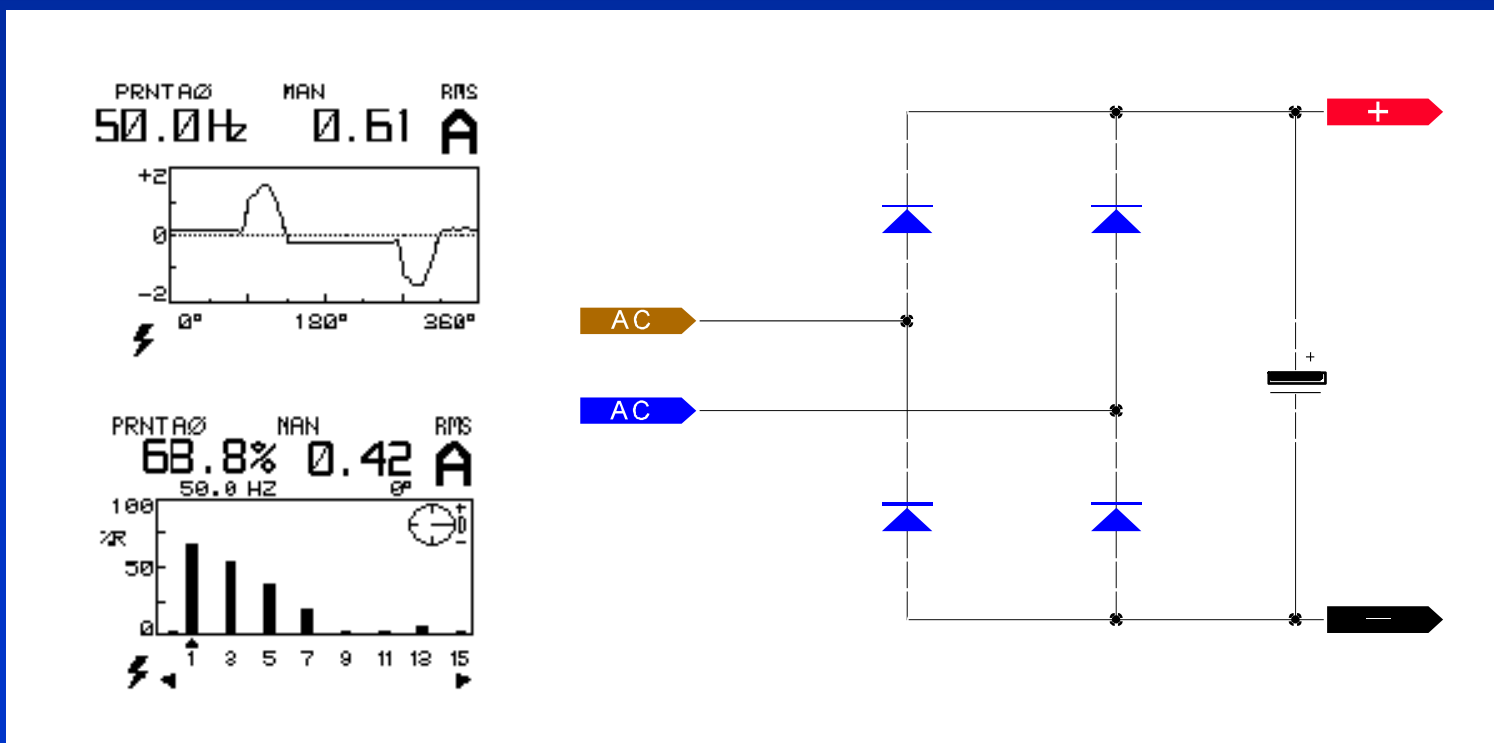
## Non-Linear Currents

→ Currents with large levels of harmonics present are drawn mainly from rectifiers with output smoothing capacitors.



# The Active Power Filter

---


## Problems Caused by Harmonics

- Overheating of electrical machinery
  - Increased RMS currents increase power loss in conductors.
- Interference to telecommunications
  - Most harmonics (7<sup>th</sup> upwards) are in the audible range.
- Damage to power factor correction equipment
  - High frequency currents cause excessive heating of power factor capacitors.

# The Active Power Filter
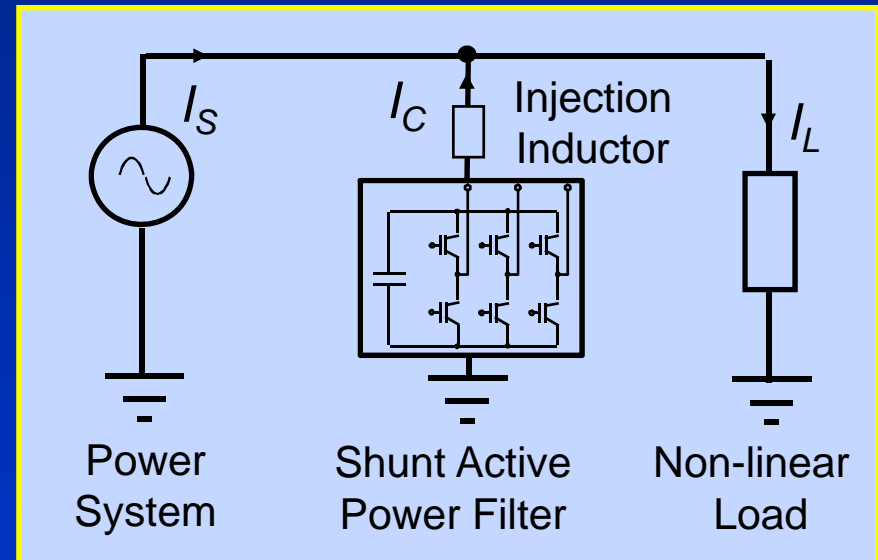
## System Diagram


- A site draws a non-linear load current.
- This current contains harmonics.
- The Active Power Filter injects harmonic currents that cancel those drawn by the load.



# The Active Power Filter
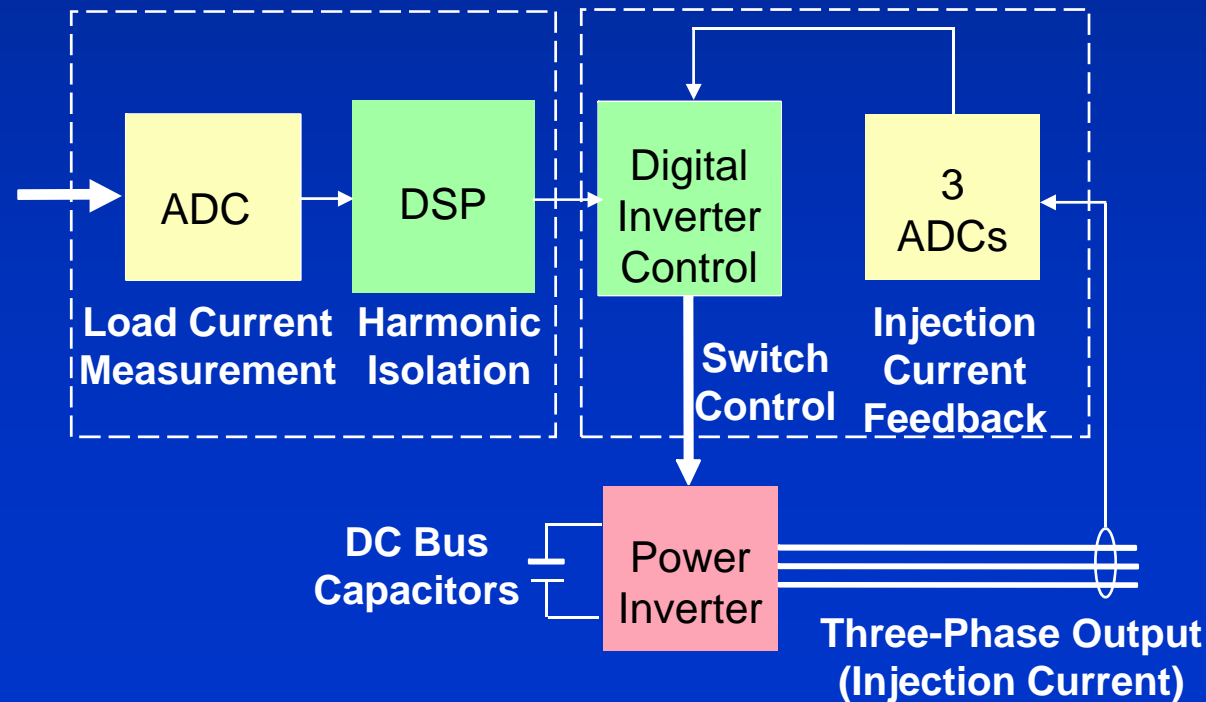
## Elements of the Active Power Filter

- Harmonic Isolation
- Current Controller for the Inverter
- Three-phase power inverter




# Hysteresis Current Control
 
## Principle of Operation

The current is ramped up and down through an inductor so that it follows a reference waveform.


The hysteresis band is twice the hysteresis limit.



# Hysteresis Current Control
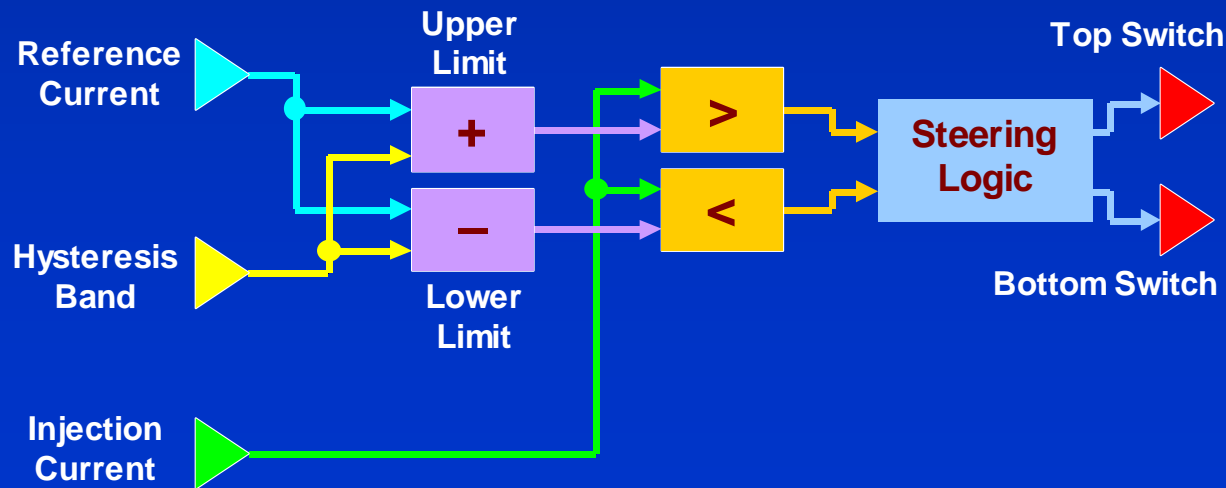
## Digital Inverter Control


- The hysteresis limits are generated with digital adder/subtractors.
- The comparison of the injection current to the hysteresis limits is performed digitally by “2’s Complement” magnitude comparators.



# Hysteresis Current Control
 
## Field Programmable Gate Arrays (FPGAs)

- Used to implement the Digital Inverter Controller.
- FPGAs contain many logic blocks that are interconnected with memory cells and can be modified without changing the circuit board.
- A single FPGA can be equivalent to thousands of logic gates.



“Floorplan” of the Xilinx 4005E FPGA with the Inverter Controller



# Inverter Requirements

---

## Injection Inductor

- The injection inductor must be chosen so:
  - The current can change fast enough to follow the high frequencies in the reference.
  - Be large enough to make the average switching frequency as low as possible to reduce losses in the inverter.
  - The maximum harmonic slope is given by:

$$\max\left(\frac{di}{dt}\right) = A2\pi f$$


- The current slope of the inductor is given by:

$$\frac{di}{dt} = \frac{\frac{1}{2}V_{DC} - V_{Supply}}{L}$$


# Inverter Requirements
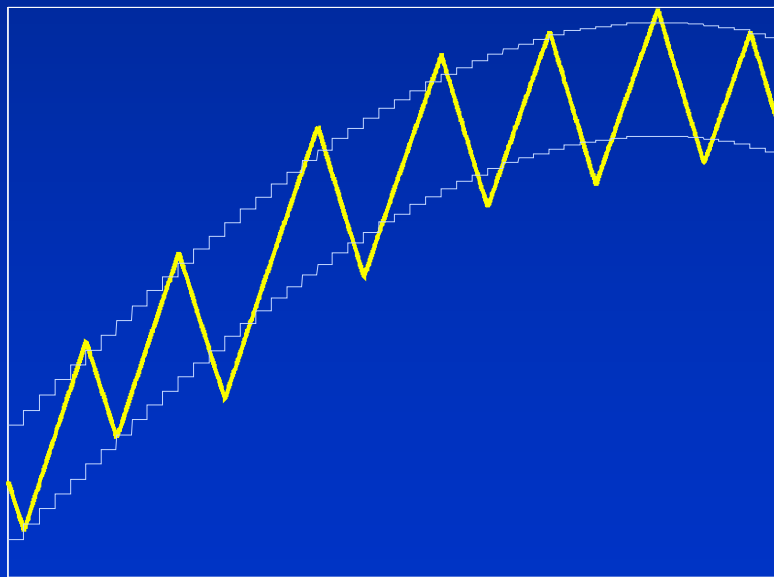
## Sampling Frequency

The digital hysteresis controller makes decisions at fixed times, rather than continuously as an analogue controller does. The more often a decision is made, the less current overshoot.




$$f_{\text{sample}} = 10\text{kHz}$$

 

$$f_{\text{sample}} = 200\text{kHz}$$


# Inverter Controller Design
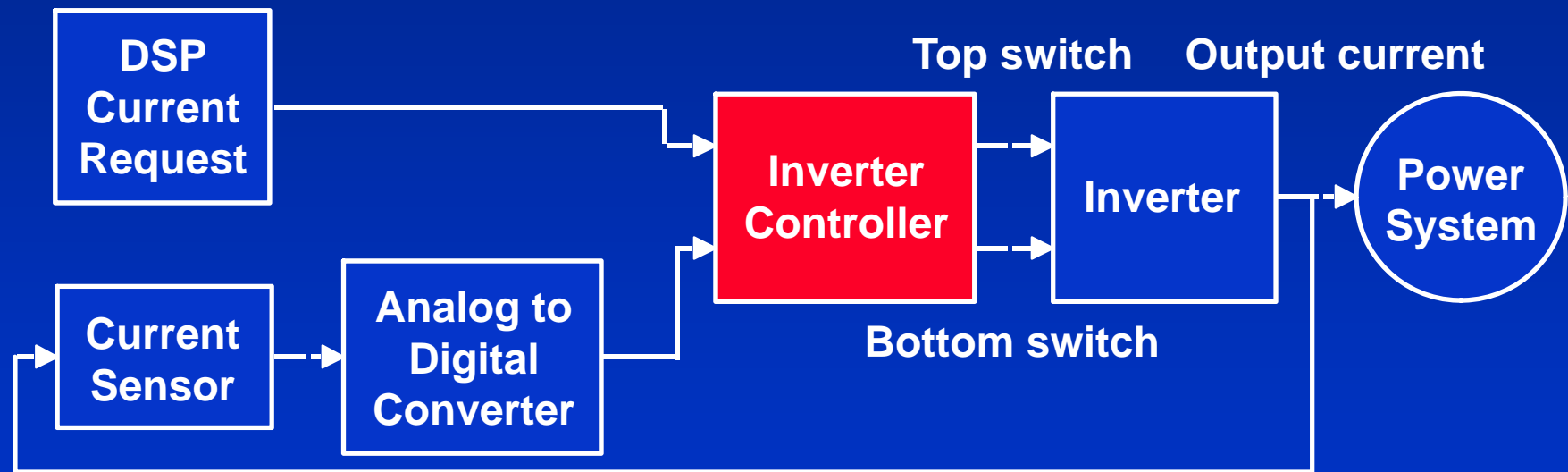
## Inverter Controller System Diagram (One of three phases)



# Inverter Controller Design

## Inverter Controller Block Diagram

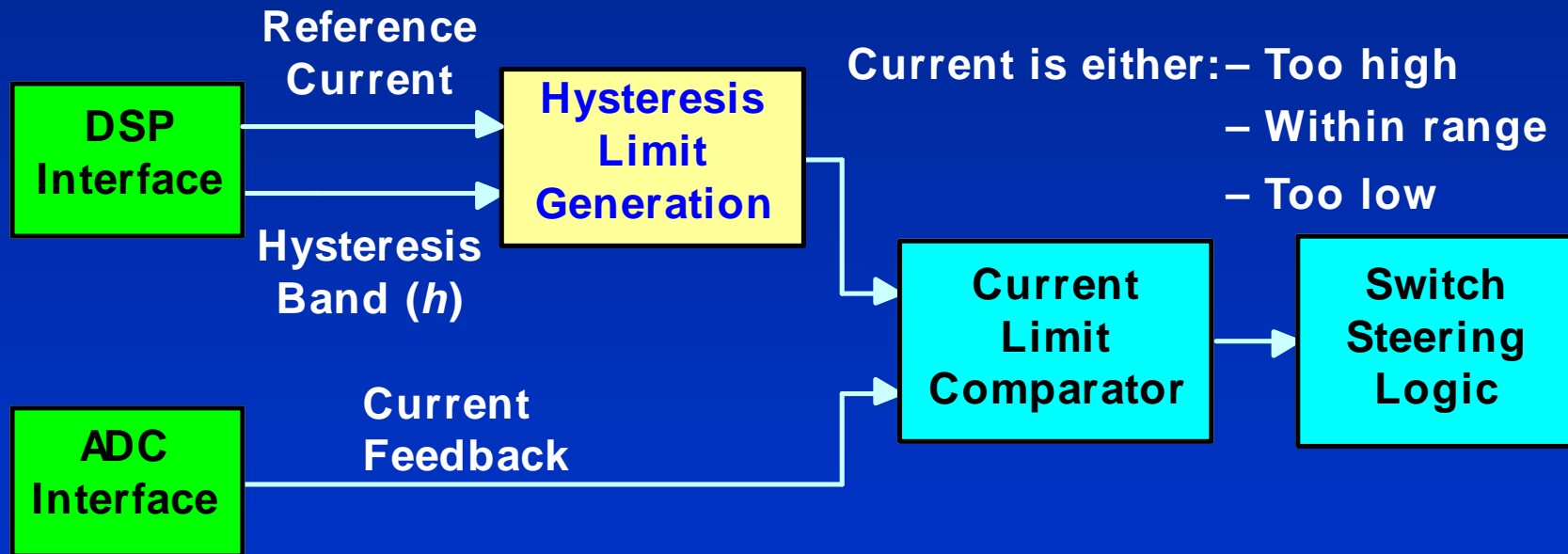

# Inverter Controller Design

## Parameter Selection

- 400A<sub>PEAK</sub> load with precision to 0.2A requires 4000 'points'. This requires 12 bit analogue to digital converters.
- Limit the current overshoot to 5A for an 800μH inductor with an 800V<sub>DC</sub> bus,

$$\Delta i_{Over} = \frac{\frac{1}{2} V_{DC}}{L} \frac{1}{f_{Sample}}$$


indicates that  $f_{sample}$  must exceed 100kHz. 260kHz is the used for the feedback ADCs — this is as fast as possible for the ADC used.

# Experimental Results

## Test Inverter

800V, 12A<sub>PEAK</sub> IGBTs

$V_{DC}$  is 60V

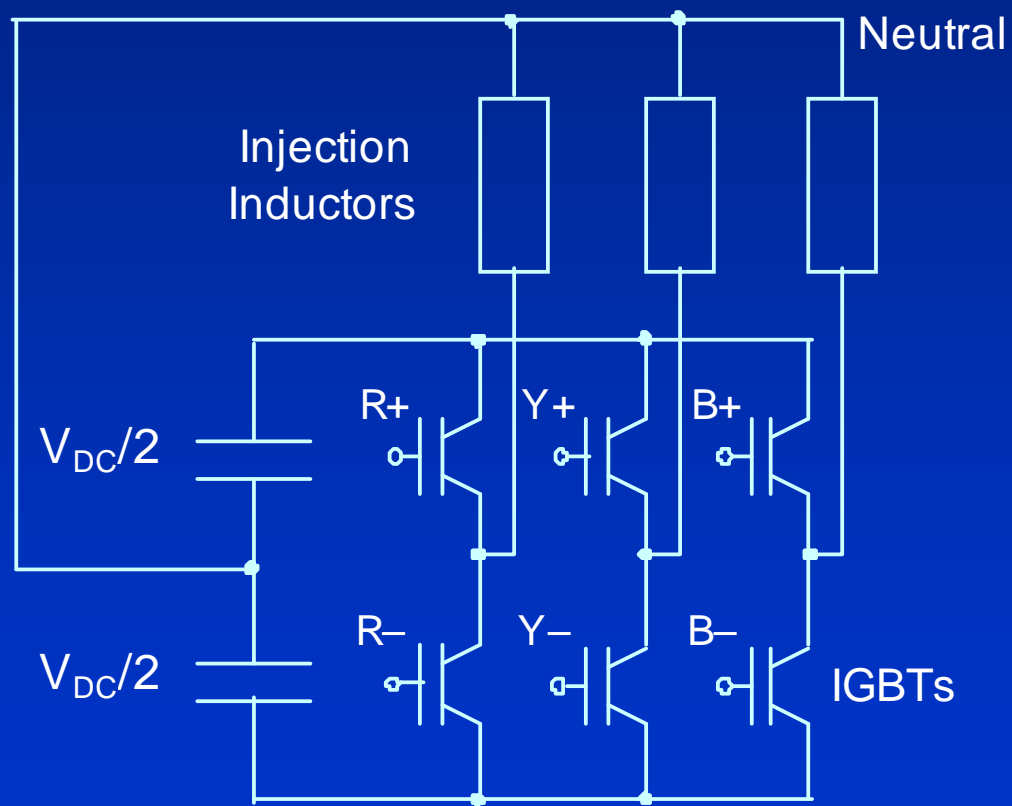

# Experimental Results


## Three-Phase Output

55Hz Output

$2A_{PEAK}$

$h = 0.5A$



$L=9mH$

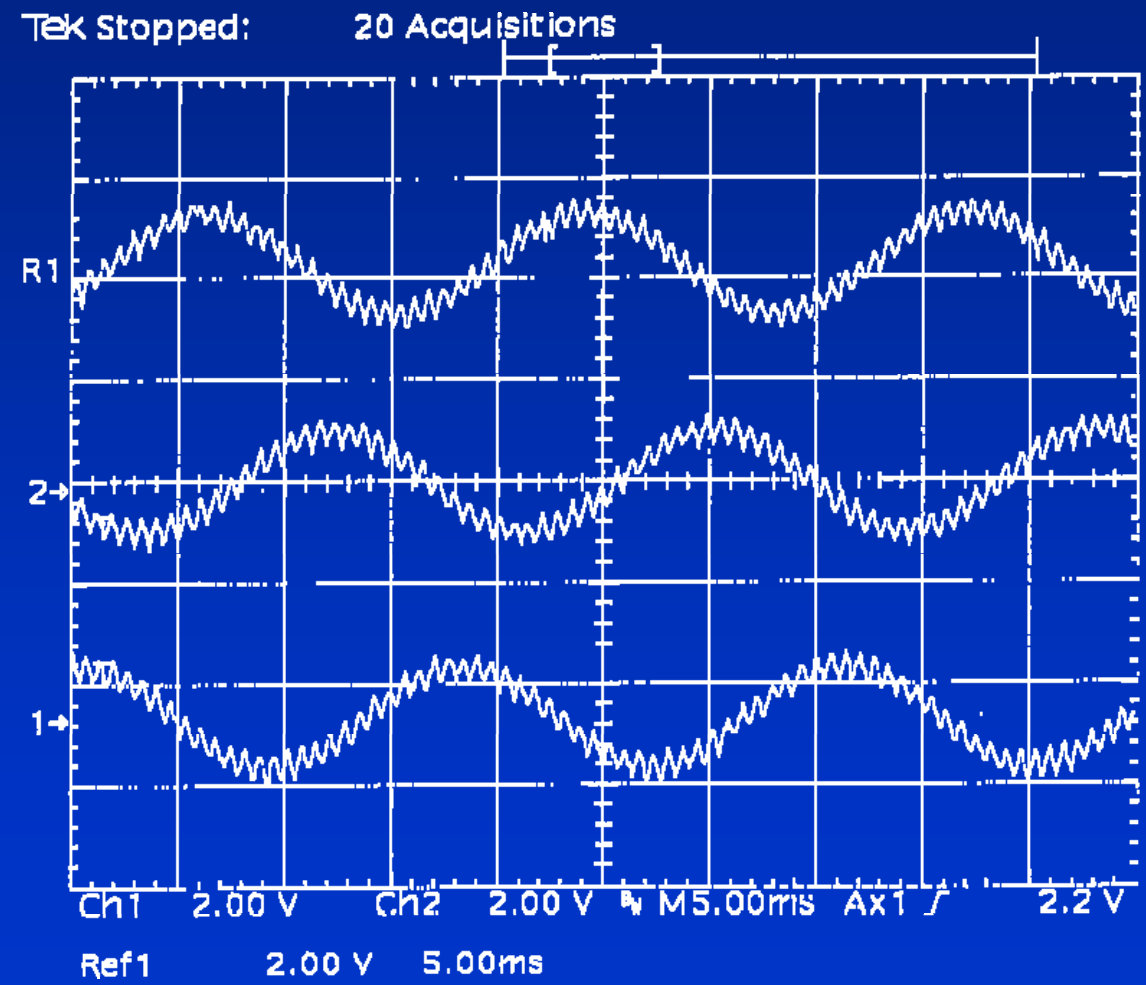

# Experimental Results
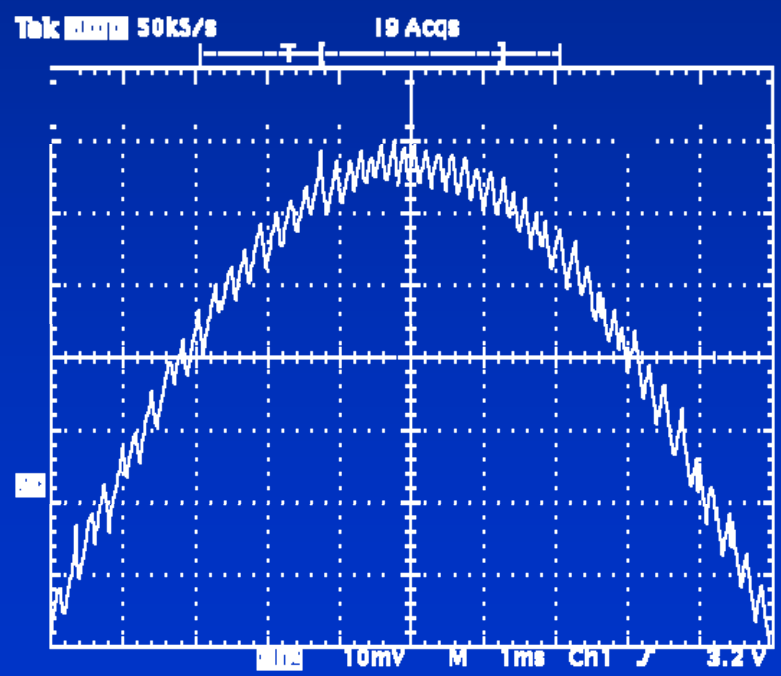 
## Sinusoidal Outputs

The inverter output is a 36Hz 4.24A<sub>RMS</sub> sinewave with  $\Delta I=0.2A$ . An injection inductance of 9mH was used. The switching noise peak is at 4.65kHz and the magnitude of the noise is 2% of the fundamental.







# Experimental Results

## Compensation Current Output (For three-phase bridge rectifier)

Frequency  
Domain

 


Time  
Domain

 


$L=4\text{mH}$

# Experimental Results


## Space Vector Diagrams

 


$h=0.1A$      $h=0.2A$

 

All currents are  
100Hz,  $3A_{PEAK}$

 


$h=0.3A$      $h=0.6A$

 

# Experimental Results

## Analogue Noise

 

High frequency noise is present at the inputs to the ADCs.

Any noise introduced at this point stays in the system and reduces the effective resolution of the ADCs.

# Digital Hysteresis Control

---

## Field Programmable Gate Array Implementation

- Interfaces directly to a digital signal processor
- Highly resistant to RF interference
- Very flexible control
  - The Hysteresis Band is easily changed on the fly, allowing constant frequency hysteresis control to be implemented at a later stage.
  - Very little trimming of analog components required (only the analogue to digital converters).
- Compact design that can be easily modified at a later stage without changes to board layout.

# Conclusions

---

- A novel digital hysteresis controller has been implemented in a Xilinx FPGA and tested with a small-scale three-phase inverter.
- Current overshoots that are not present in analogue controllers result from discontinuous sampling.
- Immunity to interference is far higher due to the digital representation of the compensating current.
- An field programmable gate array implementation:
  - Is easily interfaced to digital signal processors,
  - Is compact,
  - Allows the design to be updated without changing the circuit board.

# Acknowledgments

---

Many thanks to:

- Metalect Industries (NZ) Ltd
- Telecom Corporation of New Zealand
- Maxim Integrated Products
- National Semiconductor Corporation